

FSM Design Review

FSM Design

- Simple example in class to demonstrate design strategy and coding styles
 - Example: Traffic Light Controller
 - Sequence “Green – Amber – Red – Green – Amber ...”
 - Duration of each light is on should vary
-

Design Process

- Decide inputs and outputs
 - Input: use counter to control state transitions
 - Output: must control lights and state duration
- Decide states, control of state transitions and outputs
 - Moore or Mealy?
 - Document in state graph or ASM

Draw your own state graph now!

Design Process

- Decide inputs and outputs
 - Input: use counter to control state transitions
 - Output: must control lights and state duration
- Decide states, control of state transitions and outputs
 - Moore or Mealy?
 - Document in state graph or ASM


Moore State Graph:

Input:


- cnt_done (Flag from counter block to move state)

Outputs:

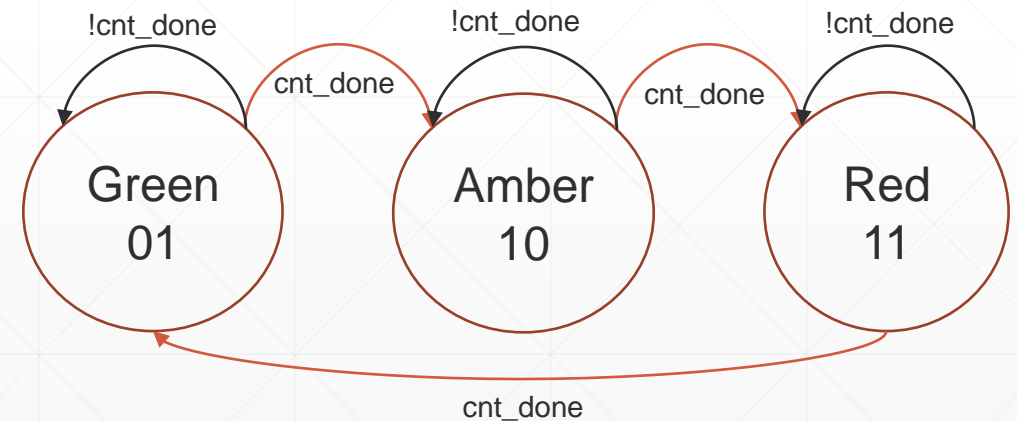- current_state (01 = green, 10 = Amber, 11 = Red)



Algorithmic State Machine (ASM)

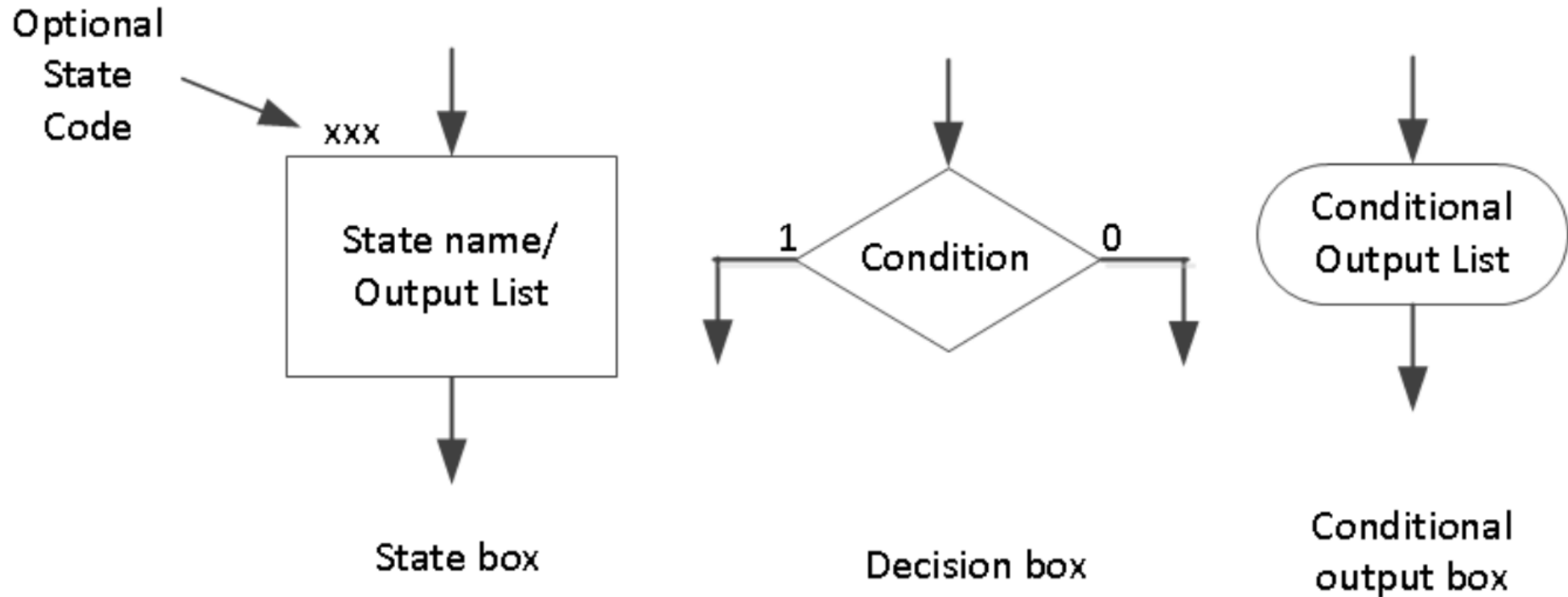

<https://www.xilinx.com/support/documentation/university/Vivado-Teaching/HDL-Design/2015x/VHDL/docs-pdf/lab11.pdf>

Page 2

In-Class Demo: FSM Example Code and Basic Testbench

- Coding style – can choose to separate next state logic and output definitions
- Registering outputs
 - Why is this a good general coding practice?