

# Digital Design Review


---

## Lecture 1

# Overview

- Digital design flow
- Synchronous sequential logic circuits vs combinational logic circuits
- Verilog recap
  - Language features and syntax
  - Registers vs Latches
  - Coding style
- The Verilog Simulator
- Design Example

# The Digital Design Flow (FPGA)

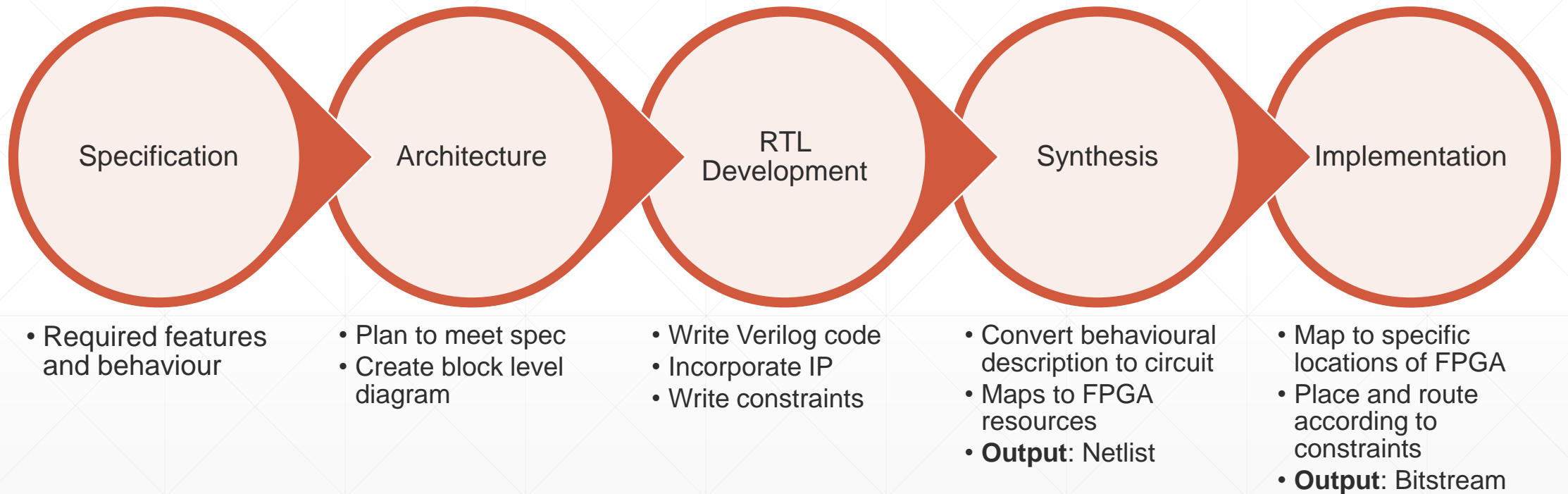

## How would this differ for ASIC?


# Digital Logic Types

- Combinational/ Asynchronous logic:
  - Outputs of the circuit rely only on current inputs
- Sequential logic:
  - Outputs of the circuit can depend on current inputs and history of inputs
  - Uses feedback
- Synchronous logic:
  - Controlled by a clock signal, changes in circuit are aligned to a clock edge

# Digital Logic Types

 
## Example components of: Synchronous Sequential

- Finite State Machine (FSM)
- First In First Out (FIFO) memory



## Example components of: Combinational

- OR gate
- Buffers
- Adder

 

- Module definition & instantiation
- Data types and declarations
  - Implicit declaration
- Operators
  - Logic
  - Arithmetic
  - Assignment
- Synchronous always block
- Combinational always block
- Conditional syntax
  - if, case, ternary statement
- Avoiding latches

## Verilog Recap

---

Primarily focusing on Verilog-2001 syntax.

All Verilog-2001 can be compiled as SystemVerilog.

Some SystemVerilog features will be mentioned, but **SV-only code syntax is not examinable**

# Module Definition and Instantiation

## Module definition

```
module module_name (  
    input          a,  
    input          [1:0] b,  
    output         c,  
    output reg     d  
);  
endmodule
```

## Module instantiation

```
module_name instance_name (  
    .a(sig1),  
    .b(sig2),  
    .c(sig3),  
    .d(sig4)  
);
```

# Data Types

- Standard types: **wire**, **reg**, **integer**
  - Systemverilog adds **logic** type
- 4 state types for synthesizable types: '0', '1', 'x', 'z'
- **What does it imply if a signal has a value of z?**
  - 1: Value is too large to display
  - 2: Negative value assigned to unsigned data type
  - 3: The signal is disconnected
  - 4: The signal value is unknown




# Data Types

- Many synthesizable types... **wire**, **reg**,
  - Systemverilog adds **logic** type
- 4 state types for synthesizable types: '0', '1', 'x', 'z'
- Other types primarily used for parameters and/or simulation
  - int, real
- Implicit declaration type is one bit wide
  - Verilog won't warn you if you assign without a declaration!
  - `assign my_undeclared_signal = 4'b1110;`
- Literal format is <bit width>'<base><value>
  - `4'b111`, `4'd15`, `4'hf`, `4'o17`
 
# Data Types – Vectors and Arrays

- Vector definition, SV “packed” dimension
  - `reg [7:0] a;`
- Array definition, SV “unpacked” dimension
  - `wire b [1:0];`
- Can have multiple dimension arrays:
  - `wire [7:0] c [1:0];`
  - `reg [7:0] d [3:0] [1:0];`
- Index value is arbitrary
  - `reg [6:-1] a;`
- Index definition is pretty flexible...
  - `reg [7:0] d [0:3] [2];`
- Be consistent!



# Operators

- Two versions of AND, OR, NOT:
  - Logical operators `&&`, `||`, `!`
  - Bit-wise operators `&`, `|`, `~`
  - Equality `==`
  - Using the wrong type can be difficult to debug... Choose wisely!
- Arithmetic operators
  - `+`, `-`, `*`, `/`, `**`
- Shift operators
  - Unsigned `>>`, `<<`,
  - Signed `>>>`, `<<<`
- Assignment operators: `=`, `<=` ...

# Synchronous Logic

## Verilog Definition of a Flip-Flop

```
reg [3:0] count_ff, count_nxt;
always @ (posedge clk) begin
    if (reset) begin
        count_ff <= 'b0;
    end else begin
        count_ff <= count_nxt;
    end
end
```

1. reg type

2. Clocked always block

3. Reset behaviour

4. D to Q assignment

5. Only <= used (NBA)

# Synchronous Logic With Asynchronous Reset

```
reg [3:0] count_ff, count_nxt;  
always @ (posedge clk, negedge reset_n)  
    if (!reset_n) begin  
        count_ff <= 'b0;  
    end else begin  
        count_ff <= count_nxt;  
    end  
end
```

1. reg type

2. Clocked always block

3. Reset behaviour

4. D to Q assignment

5. Only <= used (NBA)

## Quick Poll: Is this reset 1) active high or 2) active low?

# Strict Coding Rules for Synchronous Logic

- Every register to be inferred uses
  - `_nxt` for combinatorial next value
  - `_ff` to denote registered value
- Clocked Process
  - Registered value `_ff` only updated in clocked always block
  - No other logic in clocked block (besides reset or enable)
  - Clocked block uses non-blocking (`<=`)
  - Register input `_nxt` is assigned by combinational process...

# Combinational Logic

- Continuous assignments

```
wire up;  
assign up = 1'b1;  
assign count_nxt = up? count_ff + 1'b1 : count_ff - 1'b1;
```

- Procedural assignments

```
reg [3:0] count_ff, count_nxt;  
always @(*) begin  
    if (up) count_nxt = count_ff + 4'b1;  
end
```

- What if up is 1'b0?

# Asynchronous Sequential Logic...

## Latches

- What is a latch?
- Inferred by synthesis if combinatorial signal not defined in all cases
- Why is inferring a latch a problem?



# Avoiding Latches: Golden Rule

- *To synthesize combinational logic using an always block, **all** variables must be assigned under **all** conditions.*
- Every combinatorial always block should have default assignments

# Avoiding latches

- What is wrong here?

```
wire up, down;  
always @(*) begin  
    if (up) begin  
        count_nxt = count_ff + 4'b1;  
    end else if (down) begin  
        count_nxt = count_ff - 4'b1;  
    end  
end
```

*\*Incorrect, DO NOT COPY\**

# Avoiding latches

- Avoid by completing if statement:

```
wire up, down;  
always @(*) begin  
    if (up) begin  
        count_nxt = count_ff + 4'b1;  
    end else if (down) begin  
        count_nxt = count_ff - 4'b1;  
    end else begin // final else to avoid latch  
        count_nxt = count_ff;  
    end  
end
```

# Avoiding latches

- Avoid by using default case item in case statements:

```
always @(*) begin
    case ({down, up})
        2'b01: count_nxt = count_ff + 4'b1;
        2'b10: count_nxt = count_ff - 4'b1;
        default: count_nxt = count_ff;
    endcase
end
```

# Avoiding latches

- Avoid by using default assignments:

```
always @(*) begin
    count_nxt = count_ff;
    if (up)    count_nxt = count_ff + 4'b1;
    if (down)  count_nxt = count_ff - 4'b1;
end
```

# Verilog is a Hardware Description Language

**REMEMBER:** How descriptions are interpreted is subjective.

```
reg [3:0] count_ff, count_nxt;

always @ (posedge clk) begin
    if (reset) begin
        count_ff <= 'b0;
    end else begin
        count_ff <= count_nxt;
    end
end

always @ (*) begin
    if (enable) begin
        count_nxt = count_ff + 4'd1;
    end else begin
        count_nxt = count_nxt;
    end
end
```

# Think about your resources when designing logic

A standard D-flop will exist in almost any library.

```
always @ (posedge clk or posedge reset) begin
    if (reset) begin
        reg_ff <= 'b0;
    end else begin
        reg_ff <= reg_in;
    end
end
```

But not all configurations will exist. For example Xilinx FPGA registers can do either async set or async reset but not both at the same time.

```
always @ (posedge clk or posedge set or posedge reset) begin
    if (reset) begin
        reg_ff <= 1'b0;
    end else if (set) begin
        reg_ff <= 1'b1;
    end else begin
        reg_ff <= reg_in;
    end
end
```

# Strict Coding Rules

- Separate the combinatorial process(es)
  - All `_nxt` values assigned in always `@(*)` block, never assign `_ff` types here
  - Only use blocking assignments (`=`)
- A variable can only be assigned value by single process
  - What happens if multiple always `@(*)` blocks assign to one variable?
- All variables given value in all paths in code, avoid latches



# Strict Coding Rules

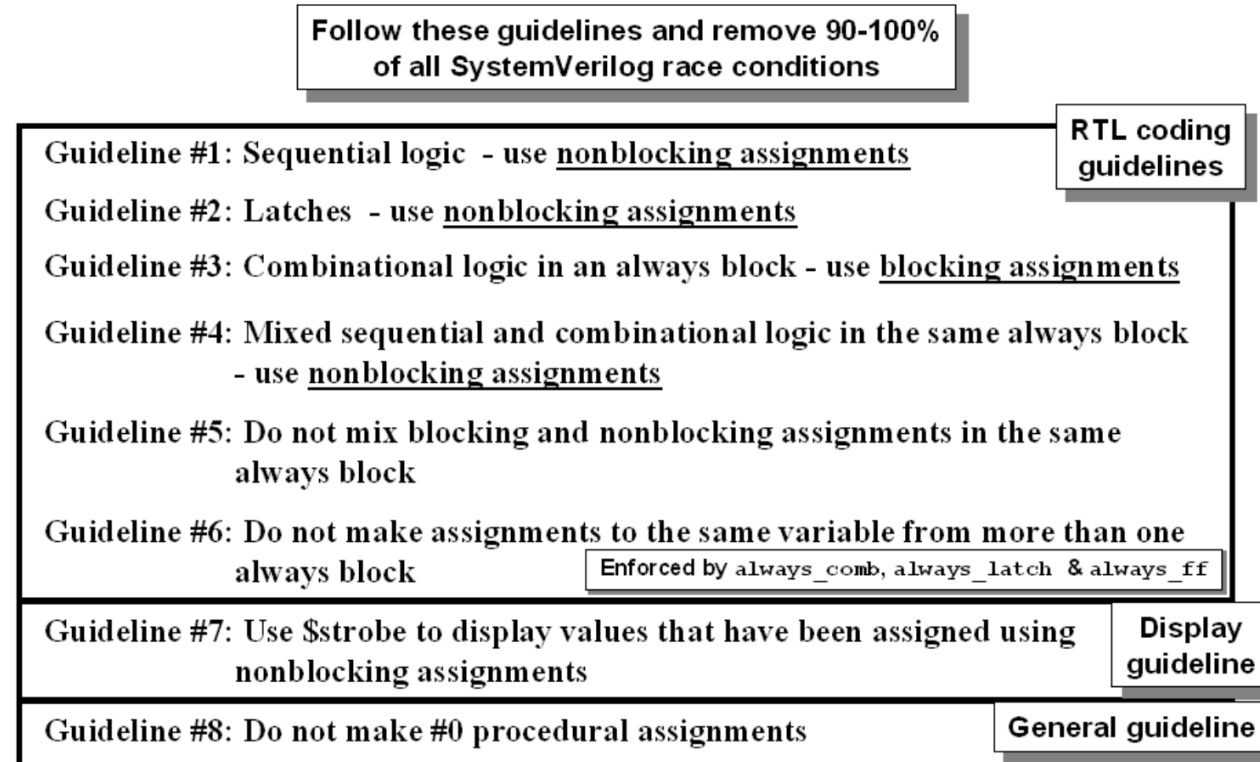


Figure 3 - Sunburst Design's - 8 Coding Guidelines to Avoid Verilog Race Conditions

# Strict Coding Rules

- These apply to describing hardware-synthesisable Verilog only
- Will see non-synthesisable code constructs for testbench use only...
- In the case of non-synthesisable code these rules do not all apply.


# Other Useful Verilog Constructs...

- Constants: localparam, parameter
- generate
- function & task
- for loop, while loop
- New with SV (useful but NOT required for this course):
  - enum & typedef, struct, interface, always\_ff & always\_comb

# Verilog Simulator

Source for diagram [here](#)

Further reading [here](#)

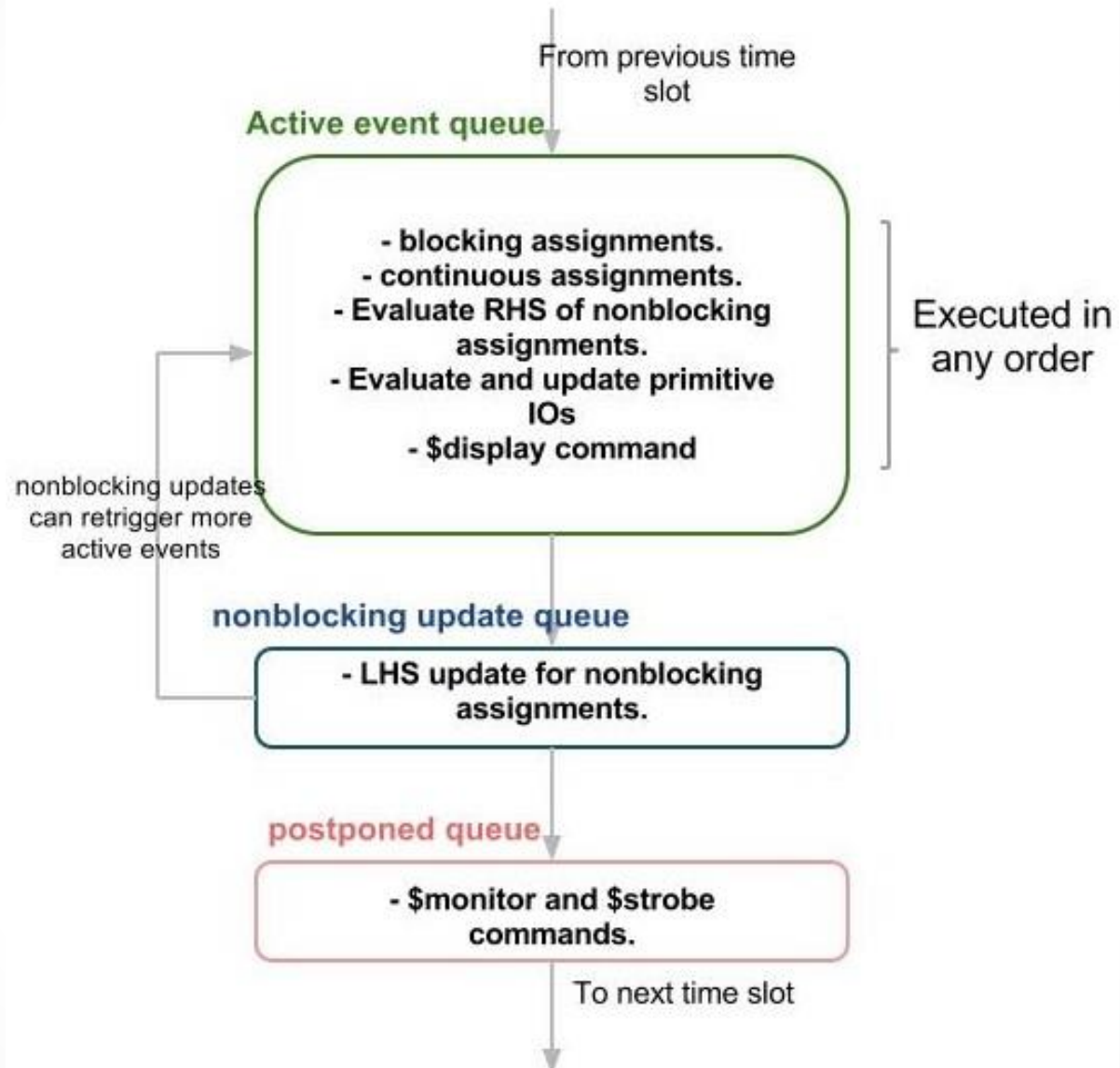

# Non-Blocking vs Blocking

## Which should be used to describe shift register?

### Option 1: Non-Blocking Assignment

```
shift_reg[0] <= in;  
shift_reg[1] <= shift_reg[0];  
shift_reg[2] <= shift_reg[1];
```


### Option 2: Blocking Assignment

```
shift_reg[0] = in;  
shift_reg[1] = shift_reg[0];  
shift_reg[2] = shift_reg[1];
```

# NBA vs BA
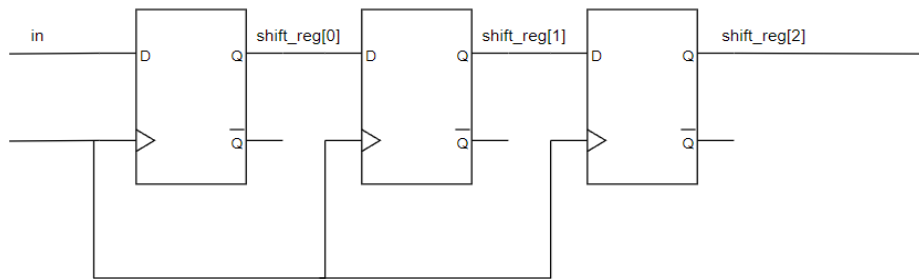
## Shift register using nonblocking assignment

```
always@(posedge clk)
begin
  if(reset) begin
    shift_reg[2:0] <= 3'd0;
  end else begin
    shift_reg[0] <= in;
    shift_reg[1] <= shift_reg[0];
    shift_reg[2] <= shift_reg[1];
  end
end
```



## Shift register using blocking assignment

```
always@(posedge clk)
begin
  if(reset) begin
    shift_reg[2:0] = 3'd0;
  end else begin
    shift_reg[0] = in;
    shift_reg[1] = shift_reg[0];
    shift_reg[2] = shift_reg[1];
  end
end
```

