

Common digital structures

Lecture 5

Common digital structures


- Digital designs are made up of simple logic cells.
- But those cells can make larger structures that are just as commonly used in digital design.
- In industry you will often find yourself re-using previously designed blocks or parts of blocks

Level to pulse


- Often control signals can be input as a constant level to indicate status.
- But often our logic expects a single clock pulse to trigger events.
- How can we make this conversion?

Level to Pulse

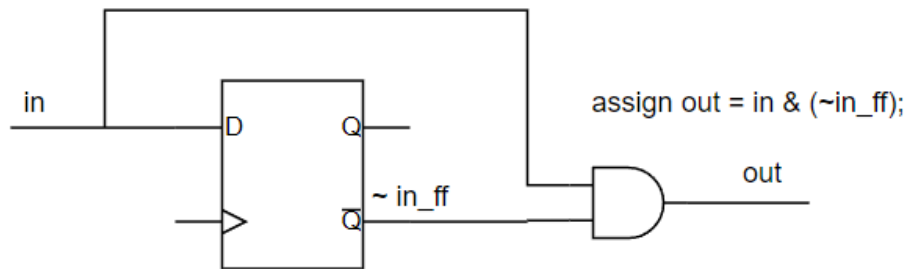- Rising edge detection
- Input has gone high but delayed version is still low.




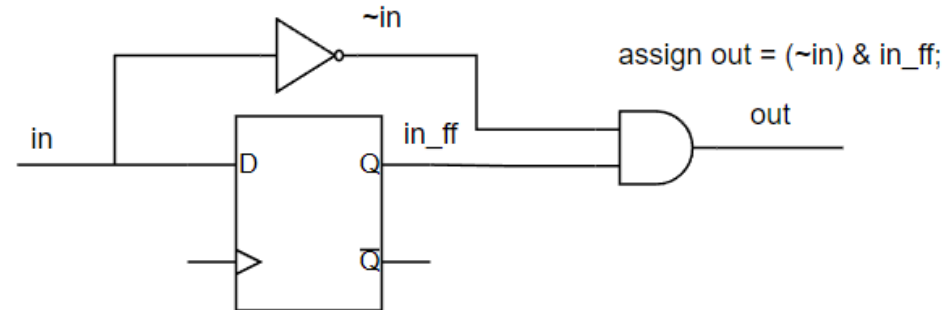- Falling edge detection
- Input has gone low but delayed version is still high.



Level to Pulse

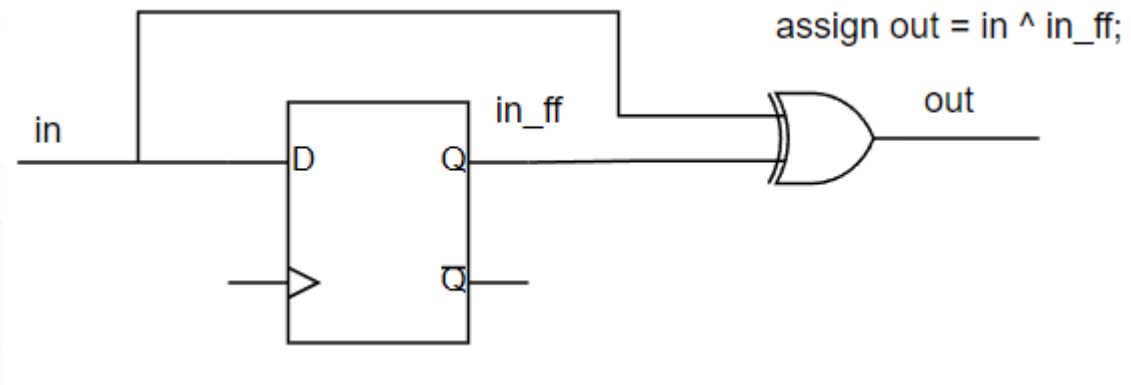- Any edge detection
- Input and delayed version are different




Real world scenarios in the digital domain


- Most of what we think of in digital design is idealized
- RTL simulations have zero delay and even asynchronous signals will driven in a synchronous way.
- This leads to a situation where poor design can generate very serious bugs which may not be found in simulation.
- So what sort of scenarios can cause these issues, and how do we catch them/ design around them?

Pulse to level

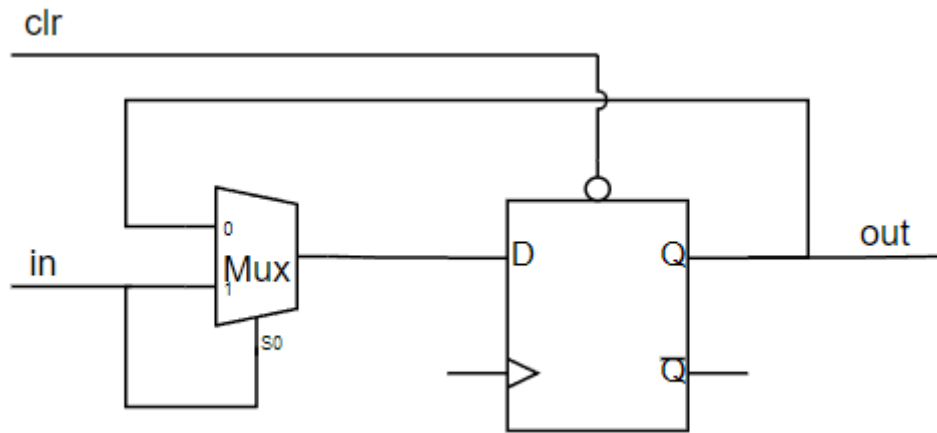- Input is “latched”* into register.
- Clear signal is required to drop level



 - Input pulse toggles register.
- No clear signal required




Reset synchronization

- In ASICs we use asynchronous resets
- Does this cause any sort of issue?


Reset synchronization
 
```
reg [3:0] aresetn_meta, aresetn_sync;  
always @ (posedge clk or negedge aresetn) begin  
    if (!aresetn) begin  
        aresetn_meta <= 'b0;  
        aresetn_sync <= 'b0;  
    end else begin  
        aresetn_meta <= 1'b1;  
        aresetn_sync <= aresetn_meta;  
    end  
end
```



ICGC (Integrated clock gating cell)
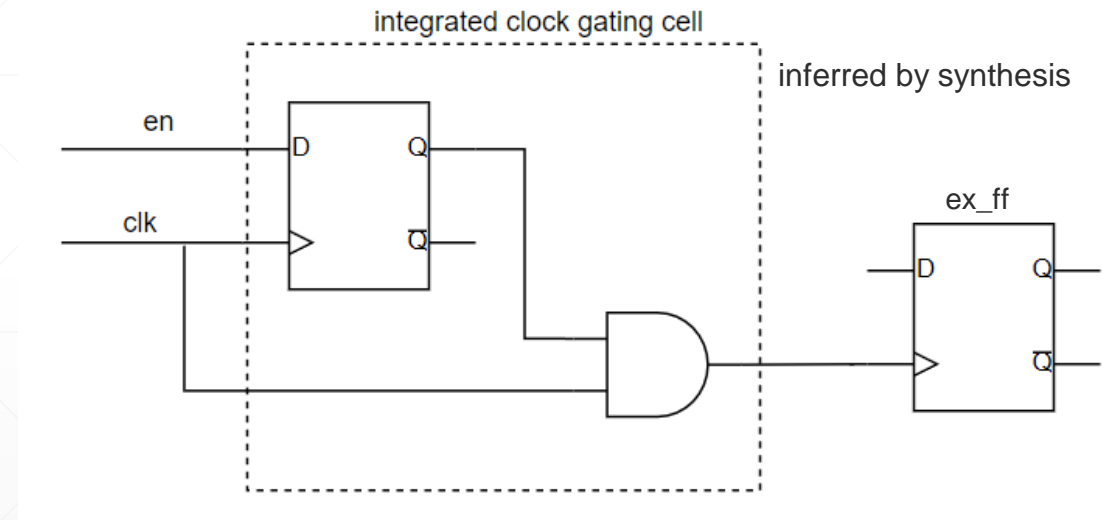
```
always @ (posedge clk) begin
    if (reset) begin
        ex_ff <= 'b0;
    end else begin
        if(en)
            ex_ff <= ex_in;
        else
            ex_ff <= ex_ff;
    end
end
```





Clock generation

- Many ICs utilize an internal oscillator, Implemented in analog which will supply the digital logic.
- Other options are externally supplied clock references.
- Often we may wish to generate extra clocks that operate at different frequencies.
- How can this be done, and how does it look on FPGA vs ASIC?

Clock Generation (FPGA)

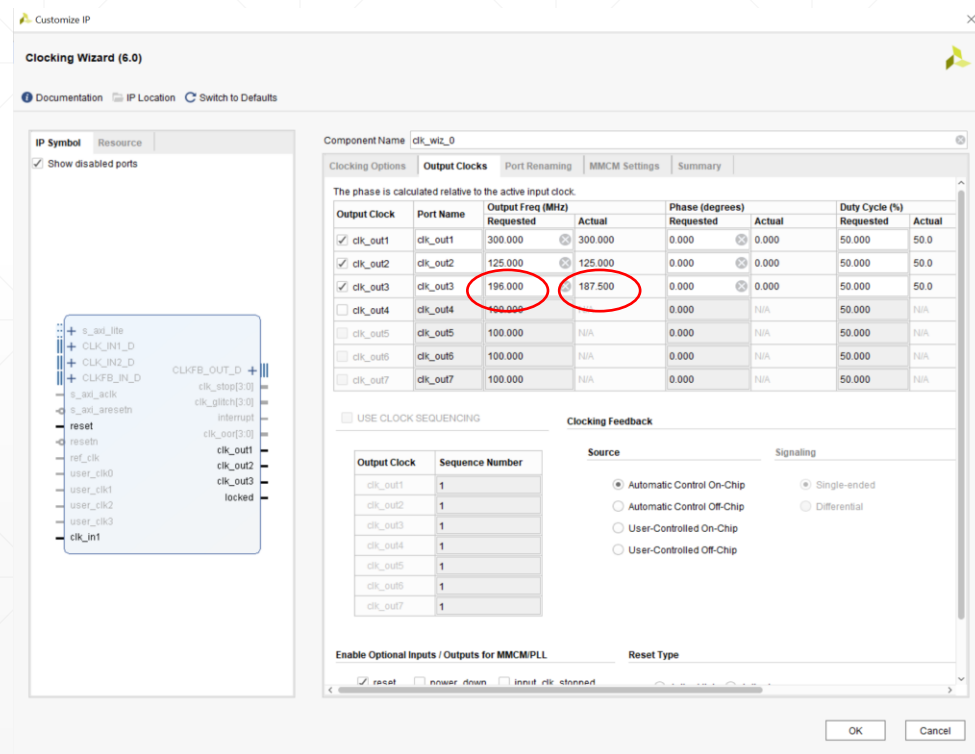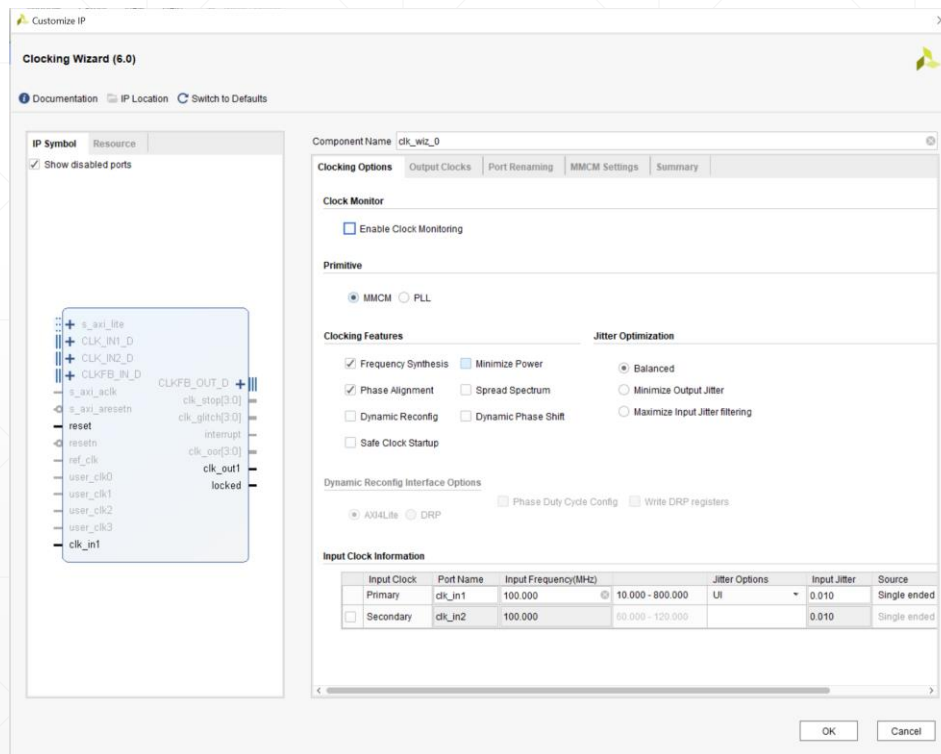- This can be done using the built in MMCM or PLL resources.
- Can be instantiated directly, but much easier to use clocking wizard IP in Vivado.
https://www.xilinx.com/support/documentation/ip_documentation/clk_wiz/v6_0/pg065-clk-wiz.pdf



Cock generation (ASIC)

- Clock divider circuit
- Clock multiplication is also possible. Requires highly characterized logic circuits.

```
reg [2:0] clk_div_cnt , aresetn_sync;  
always @ (posedge clk or negedge aresetn) begin  
    if (!aresetn) begin  
        clk_div_cnt<= 3'b000;  
    end else begin  
        clk_div_cnt <= clk_div_cnt + 1;  
    end  
end
```

```
div8_clk_en = (clk_div_cnt == 3'b111);
```

```
clk_gating_cell xclk_gating_cell(.clk_in(clk), .clk_out(clk_div8), .en(div8_clk_en) );
```

Cock generation (ASIC)

